

- ≡ Electronics Home
- ≡ Atmel ATmega16 Serial Port Example Schematic and C program
- ≡ Decoupling the power supply
- ≡ Manhattan style PCB board prototyping for high frequency RF and critical circuits
- ≡ Coil Calculator - Single-layer and mutli-layer coil calculation in javascript
- ≡ Active Bandpass Filter Javascript Tool
- ≡ Atmel AVR ATmega16 Programmer Linux
- ≡ Pic Programmer Linux
- ≡ PIC - MMC Flash Memory Extension
- ≡ PIC - 32k/64k RAM Extension

### Capacitors

Free info on Capacitors. We've done the work!

### All datasheet.com

We have the datasheet that you are searching.

### SRT Resistor Technology

Resistors for high-grade products Precision - High Value & Voltage

### Ametherm

Inrush Current Limiting Thermistors Free Samples and Application Help

Ads by Goooooogle


## Active Filter Calculator - Bandpass with OpAmp Designer in Javascript

A simple tool for designing active filters using voltage-feedback opamps.

Type in the center frequency ( $f_c$ ), bandwidth (B), gain (A) and choose a value for the capacitors (C1, C2 = C; 10nF is a good value to start) and click on "Calculate".

Light-grey fields are input fields - dark-grey fields are output fields for the calculated values.

$f_c$ =	<input type="text" value="4000"/>	Hz	Q =	<input type="text" value="12.58"/>
B =	<input type="text" value="318"/>	Hz	R1 =	<input type="text" value="30333"/>
A =	<input type="text" value="5"/>		R2 =	<input type="text" value="303326"/>
C =	<input type="text" value="3.3"/>	nF	R3 =	<input type="text" value="487"/>
<input type="button" value="Calculate"/>				

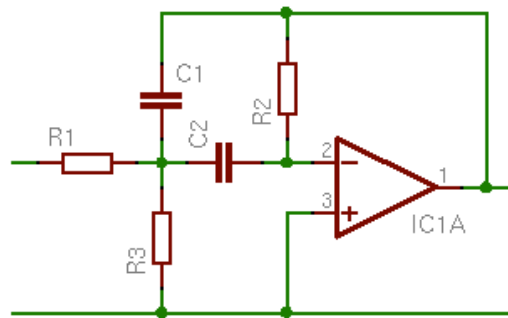

### Reverse engineer the active filter:

Use the "Resistor Series lookup" tool below to get values for available resistors and calculate the actual center frequency, bandwidth, Q factor and gain.

C =	<input type="text" value="3.3"/>	nF
R1 =	<input type="text" value="33000"/>	$\Omega$
R2 =	<input type="text" value="330000"/>	$\Omega$
R3 =	<input type="text" value="470"/>	$\Omega$
<input type="button" value="Calculate"/>		
Q =	<input type="text" value="13.34"/>	
$f_c$ =	<input type="text" value="3900.1"/>	Hz
B =	<input type="text" value="292.3"/>	Hz
A =	<input type="text" value="5"/>	

### Resistor Series lookup

Type in R in Ohm, select the series and click "Suggest"

R =	<input type="text"/>	$\Omega$
<input type="radio"/> E6 <input type="radio"/> E12 <input type="radio"/> E24 <input type="radio"/> E48		
<input type="button" value="Suggest"/>		
$R_{lower}$ =	<input type="text"/>	$\Omega$
$R_{upper}$	<input type="text"/>	$\Omega$

### Worst case frequencies:

Type in your real values of the components, select the tolerance of the capacitors and resistors and click "Calculate". The calculation will reveal the worst case center frequencies.

C =	<input type="text" value="3.3"/>	nF
Capacitors:	<input type="radio"/> 1% <input type="radio"/> 2% <input checked="" type="radio"/> 5%	
R1 =	<input type="text" value="33000"/>	$\Omega$
R2 =	<input type="text" value="330000"/>	$\Omega$
R3 =	<input type="text" value="470"/>	$\Omega$
Resistors:	<input type="radio"/> 1% <input type="radio"/> 2% <input checked="" type="radio"/> 5%	
<input type="button" value="Calculate"/>		
Values @ min. frequency:		Values @ max. frequency:
Q =	<input type="text" value="13.34"/>	Q = <input type="text" value="13.34"/>
$f_c$ =	<input type="text" value="3537.5"/>	Hz $f_c$ = <input type="text" value="4321.4"/>
B =	<input type="text" value="265.1"/>	Hz   B = <input type="text" value="323.9"/>
A =	<input type="text" value="5"/>	A = <input type="text" value="5"/>